

OLLSCOIL NA hÉIREANN, CORCAIGH
THE NATIONAL UNIVERSITY OF IRELAND, CORK
COLÁISTE NA hOLLSCOILE, CORCAIGH
UNIVERSITY COLLEGE, CORK

Summer Examination 2011

Second Science

CS2502: Logic Design


Dr Carron Shankland
Professor James Bowen
Dr Frank Böhme

Answer all questions.

90 minutes

1. Recall the two canonical forms for switching functions, i.e. the *canonical sum of products* (CSOP) and the *canonical product of sums* (CPOS). These questions deal with general properties of these two forms and their components.
 - a) Consider some switching function f about which only the following is known: Its notation in CPOS form is shorter than its notation in CSOP form (i.e. the CPOS contains fewer literals).
Which general conclusion about f can be made from the assertion above?
Hint: Consider the truth table of f . (3 marks)
 - b) Recall that *minterms* as well as *simplified products* are both *AND-combinations* of direct or inverted input variables.
Explain the general difference between these two expressions. (3 marks)

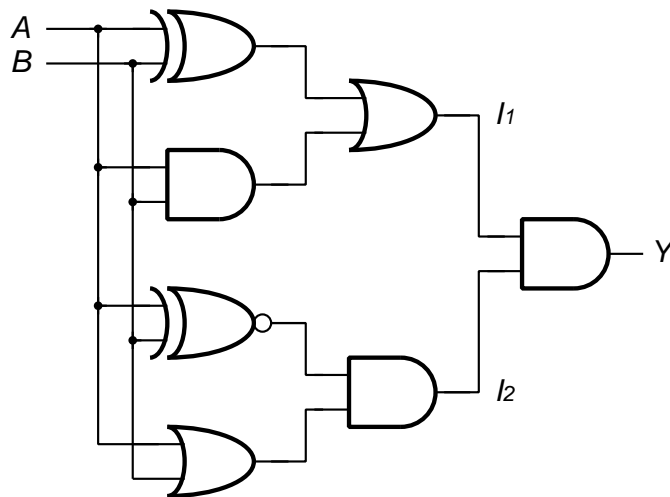2. Consider the combinational circuit given in the diagram below. The circuit contains *AND*, *OR*, *XOR* and *Equivalence* (inverted XOR) gates.




- a) Determine the shortest notation of the switching function $Y = f(A, B)$ of this circuit.
Hint: It is helpful if you first develop short notations for the two intermediate signals I_1 and I_2 . (4 marks)
- b) Could a circuit as shown in the diagram above ever be a part of a real technical device?
Justify your answer. (2 marks)

3. Recall that a typical *majority decoder* is a combinational circuit with an *odd number of inputs*. The single output Y always follows the *predominant input value*, i.e. Y assumes that value (0 or 1) that occurs on *more than half* of all input lines.

In this question, however, we consider a majority decoder with 4 inputs A, B, C, D and one output $Y = f(A, B, C, D)$. As usual, Y should follow the predominant input value, if there is any. In case of a tie, i.e. if two input lines assume 1 and two input lines assume 0, we *do not care* which value the output Y assumes.

- a) Use the a Karnaugh-map to develop an optimal SSOP form (*simplified sum of products*) of f . There are several correct solutions. (3 marks)
- b) Use the a Karnaugh-map to develop an optimal SPOS form (*simplified product of sums*) of f . There are several correct solutions. (3 marks)
- c) Develop a circuit diagram of an implementation of f that contains a *minimum number of NOR gates* and no other gates. (3 marks)
- d) Develop a circuit diagram of an implementation of f that contains a *minimum number of NAND gates* and no other gates. (3 marks)

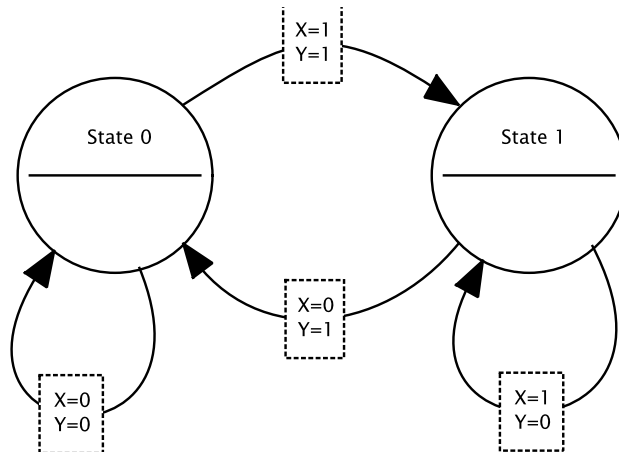4. The following questions deal with the properties of a *sequential circuit* with one binary input X , one binary output Y and two possible internal states. The state diagram of this circuit is given below.



- a) Develop all necessary tables that completely describe this sequential circuit. (4 marks)
- b) Describe the input/output behavior of this circuit in your own words. Do not use more than 3 sentences. (4 marks)
- c) Is it possible that the output remains constantly at $Y = 0$ regardless of the clock pulses? If so, which sequence of input values X causes this behavior?. (3 marks)
- d) Is it possible that the output remains constantly at $Y = 1$ regardless of the clock pulses? If so, which sequence of input values X causes this behavior?. (3 marks)
- e) How many flip-flop circuits are needed in a implementation of this circuit? (2 marks)