

**OLLSCOIL NA hÉIREANN, CORCAIGH**  
THE NATIONAL UNIVERSITY OF IRELAND, CORK  
**COLÁISTE NA hOLLSCOILE, CORCAIGH**  
UNIVERSITY COLLEGE, CORK

Summer Examination 2013

**Second Science**

**CS2502: Logic Design**

Professor Ian Gent  
Professor Barry O'Sullivan  
Dr Frank Böhme

Answer all questions.

90 minutes

1. Recall the two canonical forms for switching functions, i.e. the *canonical sum of products* (CSOP) and the *canonical product of sums* (CPOS). These questions deal with general properties of these two forms and their components.
- a) Consider some switching function  $f$  about which only the following is known: Its notation in CPOS form is a product of 50 maxterms. What is the minimum possible number of input variables (function arguments) of  $f$ ? Justify your answer. (5 marks)
  - b) Consider some switching function  $g$  about which only the following is known: Its notation in CPOS form is longer than its notation in CSOP form (i.e. the CPOS contains more literals). Which general conclusion about  $g$  can be made from the assertion above?  
Hint: Consider the truth table of  $g$ . (5 marks)
  - c) Recall that *maxterms* as well as *simplified sums* are both *OR-combinations* of direct or inverted input variables.  
Explain the general difference between these two expressions. (5 marks)
2. The questions deal with the *Associative Law*. Recall that the AND as well as the OR operations observe the Associative Law. For instance, in case of OR that law states that  $(A + B) + C = A + (B + C)$ .
- a) Does the XOR (exclusive OR) operation also observe the Associative Law?  
Justify your answer. (6 marks)
  - b) Does the NAND (NOT AND) operation also observe the Associative Law?  
Justify your answer. (6 marks)
  - c) Does the NOR (NOT OR) operation also observe the Associative Law?  
Justify your answer. (6 marks)

3. Consider a combinational circuit with 4 inputs  $A, B, C, D$  and one output  $Y$ . Its switching function expressed as the *canonical sum of products* (CSOP) is given by

$$Y = f(A, B, C, D) = m_1 + m_2 + m_3 + m_{10} + m_{11} + m_{12} + m_{14}$$

For clarification, the minterm  $m_2$  is a short notation for the product  $\bar{A} \cdot \bar{B} \cdot C \cdot \bar{D}$ .

- a) Use a Karnaugh-map to find the *simplified sum of products* (SSOP) of  $f$ . (6 marks)
- b) Rewrite your result from a) into an expression that contains only OR and NOT operations and draw the corresponding circuit diagram. This circuit diagram should only contain NOR gates. (5 marks)
- c) Rewrite your result from a) into an expression that contains only AND and NOT operations and draw the corresponding circuit diagram. This circuit diagram should only contain NAND gates. (5 marks)
- d) Use a Karnaugh-map to find a *simplified product of sums* (SSOP) of  $f$ . There are multiple possible answers. (7 marks)
4. The following questions deal with the properties of a *sequential circuit* which is given by the following specification:
- The circuit is a *Moore machine* with one binary input  $X$  and one binary output  $Y$ . The output  $Y$  depends on the two values of  $X$  sampled at the two most recent clock pulses.  $Y$  should always be the result of the NAND combination of these two input values.
- For example, let's assume we have  $X = 1$  when a clock pulse occurs. Let's assume that  $X$  has not changed when the next clock pulse occurs. Since the last two sampled values of  $X$  are 1 the output now assumes  $Y = \bar{1} \cdot \bar{1} = 0$ . Now consider the next clock pulse and let's assume that  $X$  has meanwhile changed to  $X = 0$ . This means the last two sampled input values are 1 and 0 and therefore the output now changes to  $Y = \bar{0} \cdot \bar{1} = 1$ .
- a) Draw the state diagram for this circuit. Make sure that all arcs and all states are correctly labelled.  
Hint: Your diagram should contain 4 states. However, a *Mealy machine* with similar behaviour could be realized with two states only. (6 marks)
- b) Develop the *transition table* of this sequential circuit. Make sure the rows and columns carry the correct labels. (6 marks)
- c) Is it possible to find an input sequence for  $X$  that causes the output  $Y$  to alternate with every clock pulse, i.e.  $Y = 0, 1, 0, 1, 0, 1, 0, 1 \dots$ ? If your answer is yes, then give such an input sequence. (6 marks)
- d) Is it possible to find an input sequence for  $X$  that causes the output  $Y$  to alternate with every *second* clock pulse, i.e.  $Y = 0, 0, 1, 1, 0, 0, 1, 1 \dots$ ? If your answer is yes, then give such an input sequence. (6 marks)