

Multibit Subtractor

To use a full-adder to subtract, we invert the second input (b), and set the carry-in = 1.

If we invert every b_i input in a multibit adder and set the carry-in to be 1, we have a multibit subtractor.

Combining subtraction and addition

If we take a 2–1 multiplexor and set the inputs to be b_i and $\text{NOT}(b_i)$, then the select line chooses which output goes to the multibit input.

We can then use the carry-in as the select line, and have a multiplexor for each b digit in the multibit adder/subtractor. Then setting the carry-in to be 1 gives us subtraction, and setting it to 0 gives us addition.

Some Theory

Rules of Boolean algebra

1. Closure Rule: There are 2 operators which operate on pairs of elements, producing a result belonging to the set {true, false}:
 - i. \cdot (AND)
 - ii. $+$ (OR)
2. These operators are commutative:
 - i. $A.B = B.A$
 - ii. $A+B = B+A$
3. They are distributive:
 - i. $A \cdot (B+C) = (A.B) + (A.C)$
 - ii. $A + (B.C) = (A+B) \cdot (A+C)$
4. There are two identity elements:
 - i. $1.A = A$

ii. $0+A = A$

5. For each A there is an inverse A' such that:

i. $A.A' = 0$

ii. $A+A' = 1$

Theorems

- T1: $A.0 = 0$
- T2: $A+1 = 1$
- T3: $A.A = A$
- T4: $A+A = A$
- T5: $A + (A.B) = A$
- T6: $A + (A'.B) = A+B$
- T7: $A.B.C = A . (B.C) = (A.B) . C$
- T8: $A+B+C = A+(B+C) = (A+B) + C$
- T9: $(A.B)' = A' + B'$
- T10: $(A+B)' = A' . B'$
- T11: $(A')' = A$