

OLLSCOIL NA hÉIREANN, CORCAIGH
THE NATIONAL UNIVERSITY OF IRELAND, CORK
COLÁISTE NA hOLLSCOILE, CORCAIGH
UNIVERSITY COLLEGE, CORK

Summer Examination 2010

Second Science

CS2502: Logic Design

Dr Carron Shankland
Professor James Bowen
Dr Frank Böhme


Answer all questions.

90 minutes

1. The questions deal with two well-known switching functions.

- a) Draw a circuit realization of the *exclusive OR* function (XOR) with two inputs. You may use AND, OR and NOT-gates. (2 marks)
- b) Draw a circuit realization of the *equivalence* function (EQ) with two inputs. You may use AND, OR and NOT-gates. (2 marks)
- c) Consider the two switching functions from a) and b). Give a formula that shows their relation, i.e. a formula that shows how one of these two functions can be expressed in terms of the other. (3 marks)

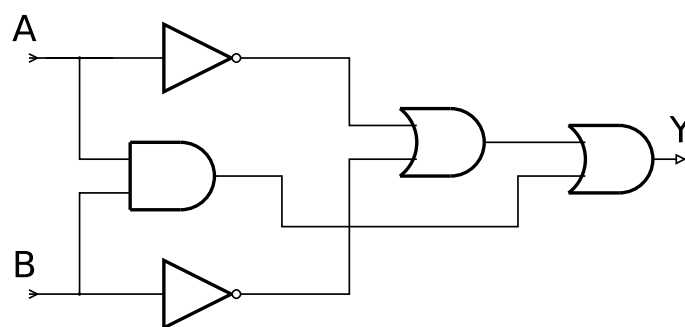2. Consider the combinational circuit given in the diagram below.



- a) Determine the switching function of this circuit. (3 marks)
- b) Could this circuit ever be a part of a real technical device? Justify your answer. (3 marks)

3. Consider a combinational circuit with 4 inputs A, B, C, D and one output Y . Its switching function expressed as the *canonical sum of products* (CSOP) is given by

$$Y = f(A, B, C, D) = m_2 + m_3 + m_4 + m_5 + m_{10} + m_{11} + m_{13} + m_{15}$$

For clarification, the minterm m_2 is a short notation for the product $\bar{A} \cdot \bar{B} \cdot C \cdot \bar{D}$.

- a) Rewrite f in CPOS form (*canonical product of sums*). You may use the short notation. (4 marks)
- b) Use your answer to a) and a Karnaugh-map to express f in SPOS form (as a *simplified product of sums*). (4 marks)
- c) Rewrite your result from b) into an expression that contains only OR and NOT operations and draw the corresponding circuit diagram. This circuit diagram should only contain NOR gates. (3 marks)
- d) Rewrite your result from b) into an expression that contains only AND and NOT operations and draw the corresponding circuit diagram. This circuit diagram should only contain NAND gates. (3 marks)
4. The following questions deal with the properties of a *sequential circuit* which is given by the following specification:
- The circuit is a *Moore machine* with one binary input X and one binary output Y . The output Y depends on the two values of X sampled at the two most recent clock pulses. Y should always be the result of the XOR combination of these two input values.
- For example, lets assume we have $X = 1$ when a clock pulse occurs. Lets assume that X has not changed when the next clock pulse occurs. Since the last two sampled values of X are *equal*, the output now assumes $Y = 0$, regardless of its previous value. Now consider the next clock pulse and lets assume that X has meanwhile changed to $X = 0$. This means the last two sampled input values are *opposite* and therefore the output now changes to $Y = 1$.
- a) Draw the state diagram for this circuit. Make sure that all arcs and all states are correctly labelled.
Hint: Your diagram should contain 4 states. However, a *Mealy machine* with similar behaviour could be realized with two states only. (4 marks)
- b) Develop the *transition table* of this sequential circuit. Make sure the rows and columns carry the correct labels. (3 marks)
- c) Give an input sequence for X that causes the output Y to alternate with every clock pulse ($Y = 0, 1, 0, 1, 0, 1, \dots$). (3 marks)
- d) Lets assume the input X changes several times *between two subsequent clock pulses*. How do such changes affect the output Y ? Justify your answer. (3 marks)