

## Adding Bits With Logic Gates (cont.)

### Example:

	1	1	1	0	1	1	0	1	
	$0_1$	$1_1$	$1_0$	$0_1$	$1_1$	$1_0$	$1_0$	$0_0$	
$C_{out} \rightarrow$	1	0		1	0	1	1	0	1
									$\leftarrow$ sum

### Truth Table for a Full Adder

We want to create a logical circuit to implement a full adder.

Lets start with the truth table:

$C_{in}$	a	b	sum	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Later we will see a mechanism for creating equations and circuits from truth tables.

For now, we are going to create a circuit by intuition and pattern-matching.

$C_{in}$	a	b	sum	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Consider the two blocks above.

In the first block  $C_{in} = 0$ , in the second  $C_{in} = 1$ .

In the first block,  $sum = aXORb$  and  $C_{out} = a.b$ , which is the same as the half adder.

In the second block,  $sum = aXNORb$  and  $C_{out} = a+b$ .

### Rewriting

If  $C_{in} = 0$ :

$$sum = aXORb, C_{out} = a.b$$

If  $C_{in} = 1$ :

$$sum = aXNORb, C_{out} = a+b$$

The following circuit implements this: (get picture)

a and b connected to each circuit listed above appropriately.

Those circuits connected to  $C_{in}$  by 2 multiplexors.

### Multiplexor:

One input to an AND can control the gate. If it's 0, the gate outputs a 0. If it's 1 the gate outputs the other input to it.

By putting an OR after two ANDs, where one input to one AND is  $C_{in}$  and one input to the other AND is  $C_{in}'$ , the value of  $C_{in}$  controls whether the result is taken from the first AND or the second AND.