

**OLLSCOIL NA hÉIREANN, CORCAIGH**  
**THE NATIONAL UNIVERSITY OF IRELAND, CORK**

**COLAISTE NA hOLLSCOILE, CORCAIGH**  
**UNIVERSITY COLLEGE, CORK**

**2015/2016**

**Semester 1 - Winter 2015**

**CS1110: Systems Organization I**

Dr Helen Purchase  
Professor C. Sreenan  
Professor J.P. Morrison

1.5 hours

Attempt all questions.  
All Questions Carry Equal Marks.  
Total Mark for this Paper is 80.  
(For information: Minutes/Mark = 1.125)

**SPECIAL REQUIREMENTS**

No electronic calculator may be used in this examination

**PLEASE DO NOT TURN THIS PAGE UNTIL INSTRUCTED  
TO DO SO  
PLEASE ENSURE THAT YOU HAVE THE CORRECT EXAM  
PAPER**

### Question 1

- a) Convert  $4410_5$  (Base 5) to Decimal, Binary, Octal and Hex. Clearly show the methods used to arrive at each answer. (4 marks)
- b) Convert the Binary number 10111 to Base 7. Clearly show the methods used to arrive at the answer. (4 marks)
- c) Convert the Octal number  $123574_8$  to Binary. Clearly show the method used to arrive at the answer. (2 marks)
- d) Convert the Hex number FACE00F to Binary and to Octal. Clearly show the methods used to arrive at each answer. (4 marks)
- e)
  - 1. Suppose a person types the characters '5', '3' and '6' on a keyboard and presses return. Outline algorithm that could be used to convert this stream of characters into the integer 536?
  - 2. If the ASCII value for the character '0' is 30 hex, what is the sequence of bytes (expressed in hex) coming from the keyboard?
  - 3. What is the minimum number of bits needed to hold the result after converting to the integer representation?(6 marks)

### Question 2

- a) Assuming 2's complement representation and just 8 bits, what is the largest positive hex number that can be represented? What decimal number do you get when you add 1 to this hex number? What number do you then get if you negate that decimal number? (6 marks)
- b) Show how each of the following can be implemented using only NOR gates:
  - 1.  $A \text{ AND } B \text{ OR } C$
  - 2.  $A \text{ XOR } B \text{ NOT } C$(8 marks)
- c) Draw the Truth-Table for a Half-Subtractor and use it to derive the equations for the Difference and the Borrow. Simplify your equations, if possible, and draw the corresponding circuit diagram. (6 marks)

### Question 3

- a) Draw a digital logic circuit diagram containing the 3 inputs: A, B and C, such that when  $C = 0$ , the output of the circuit is  $A \text{ XOR } B$  and when  $C = 1$ , the output of the circuit is  $AB$ . Finally, express this functionality as an equation (6 marks)
- b) Draw the circuit diagram for a 4-1 line multiplexor and briefly describe how it works. (6 marks)

- c) Show how function  $M = a'bc + ab'c + abc'$  could be implemented using an 8-1 line multiplexor. (4 marks)
- d) Prove the following using both Algebraic Manipulation and Perfect Induction:  
 $A + (AB) = A$  (4 marks)

#### Question 4

- a) Derive an equation for  $F$  from the following Truth-Table. Simplify the function, if possible, and use De Morgan's Theorem to convert it to NAND form only. Draw the corresponding circuit diagram. (8 marks)

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- b) Draw the circuit D-flip-flop. Using this circuit as a black-box, show how you would construct an 8-bit register and explain how it works. (8 marks)
- c) Name two special-purpose registers and describe their function. (4 marks)